

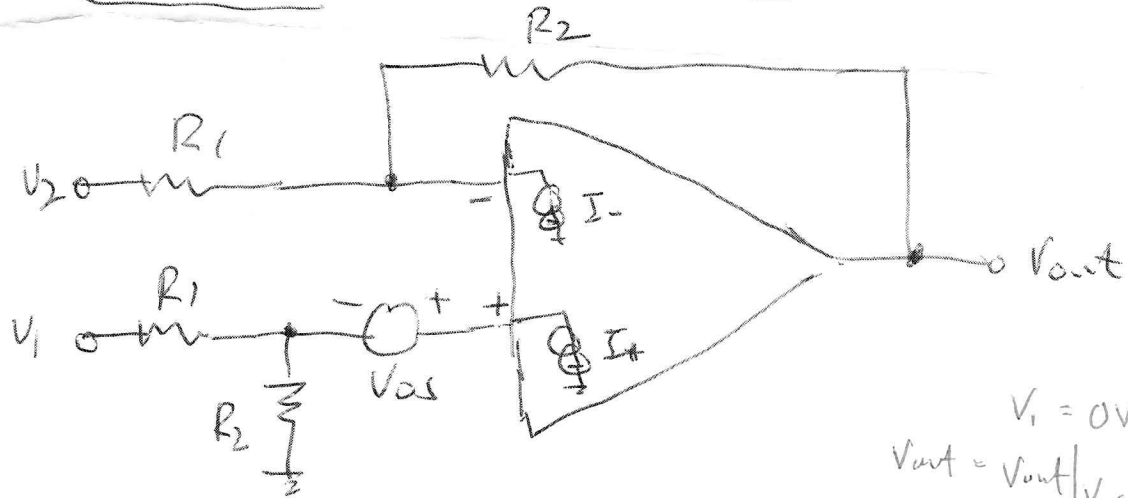
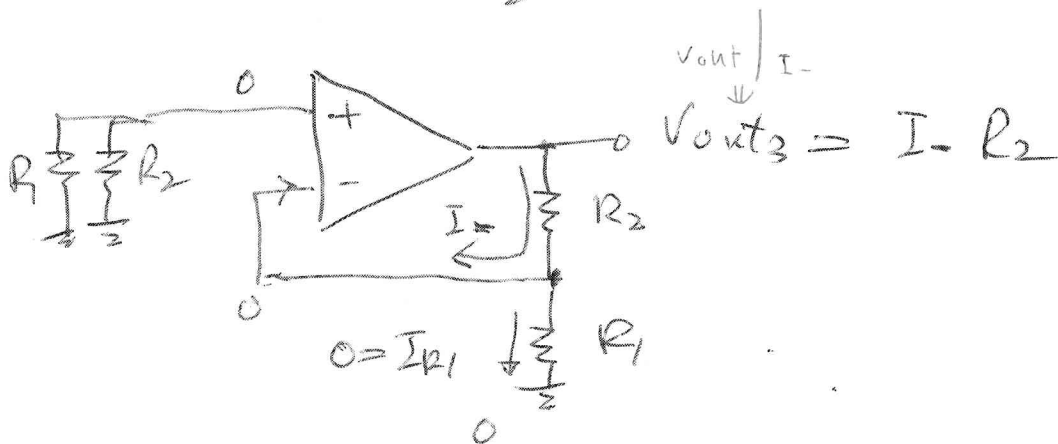


(1)

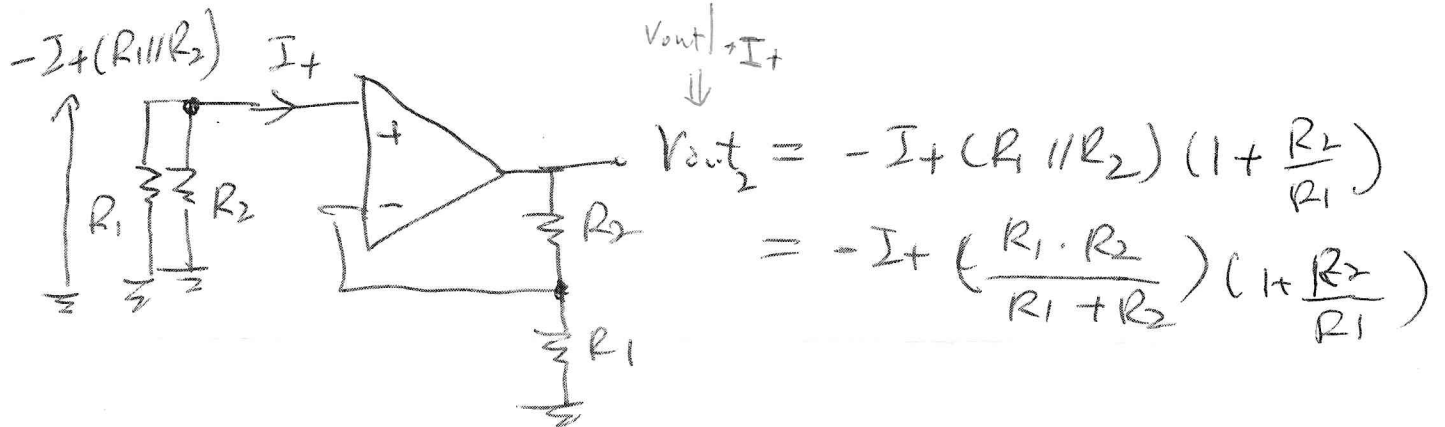

$$V_i = 0V$$


$$V_{out} = V_{out}|_{V_{os}} + V_{out}|_{I_+} + V_{out}|_{I_-}$$

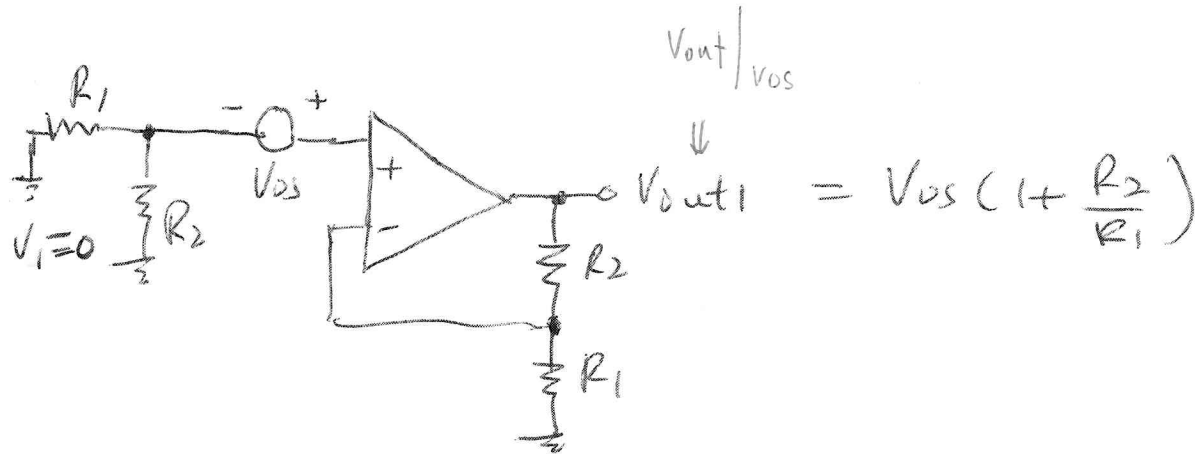

$$\therefore V_{out} = V_{out1} + V_{out2} + V_{out3}$$

2(a)

Ideal

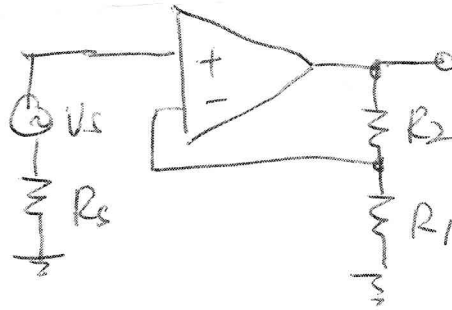


$$V_{out} = V_s \times \left(1 + \frac{R_2}{R_1}\right)$$

2(b)

Non-Ideal


$$V_c = 0$$

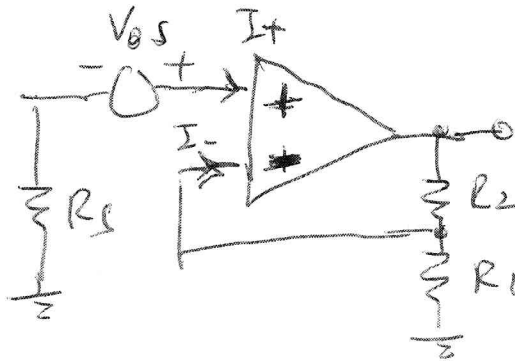

$$V_{out,dc} = V_{out}|_{I_+} + V_{out}|_{I_-} + V_{out}|_{V_{os}}$$

$$V_{out,dc} = V_{os} \times \left(1 + \frac{R_2}{R_1}\right) + (-I_+) R_s \left(1 + \frac{R_2}{R_1}\right) + (I_-) \cdot R_2$$

2(c)

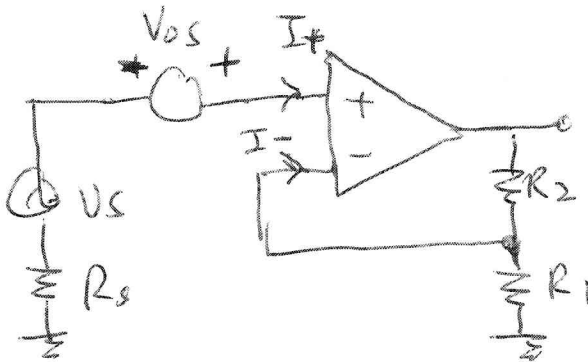

$$V_{out} = V_{out}|_{V_s} + V_{out}|_{V_{os}} + V_{out}|_{I_+} + V_{out}|_{I_-}$$

$$V_{out} = V_s \times \left(1 + \frac{R_2}{R_1}\right) + V_{os} \times \left(1 + \frac{R_2}{R_1}\right) + (-I_+) R_s \left(1 + \frac{R_2}{R_1}\right) + (I_-) \cdot R_2$$

2(d) From 2(c), $V_{out,dc} = 0$

$$\therefore 0 = V_{os} \left(1 + \frac{R_2}{R_1}\right) + (-I_+) R_s \left(1 + \frac{R_2}{R_1}\right) + (I_-) \cdot R_2$$

$$\therefore R_s = \frac{V_{os} \cdot \left(1 + \frac{R_2}{R_1}\right) + (I_-) \cdot R_2}{(I_+) \cdot \left(1 + \frac{R_2}{R_1}\right)}$$


$$\text{Given: } I_{BIAS} = \frac{I_+ + I_-}{2} = 100 \text{ nA}$$

$$I_{IO} = I_+ - I_- = -40 \text{ nA}$$

$$\frac{R_2}{R_1} = \frac{100 \text{ k}}{25 \text{ k}} = 4, \quad V_{os} = 2 \text{ mV}$$

Solve I_+ and I_- and R_s

(3)

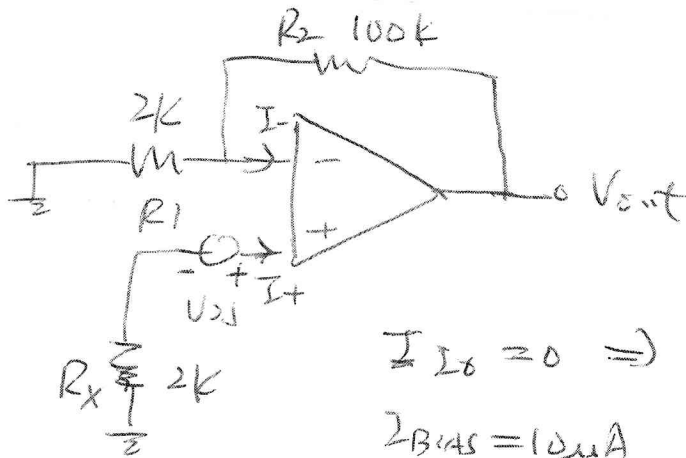

$$I_{Ios} = 0 \Rightarrow I_+ = I_- = 10 \mu A$$

$$I_{BIAS} = 10 \mu A$$

$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{os} + \left[(-I_+) \cdot R_x \cdot \left(1 + \frac{R_2}{R_1}\right)\right] + (I_-) R_2$$

(1) (2) (3)

$$= 540 mV - 1.02 V + 1.0 V$$


(1) (2) (3)

* For exact I_{BIAS} offset cancellation, (2) = (3)

$$\therefore (-I_+) \cdot R_x \cdot \left(1 + \frac{R_2}{R_1}\right) + (I_-) R_2 = 0$$

$$\Rightarrow R_x = \frac{R_1 \cdot R_2}{R_1 + R_2} = 1.96 k\Omega < 2 k\Omega$$

Slow Rate SR is independent of V_{os}

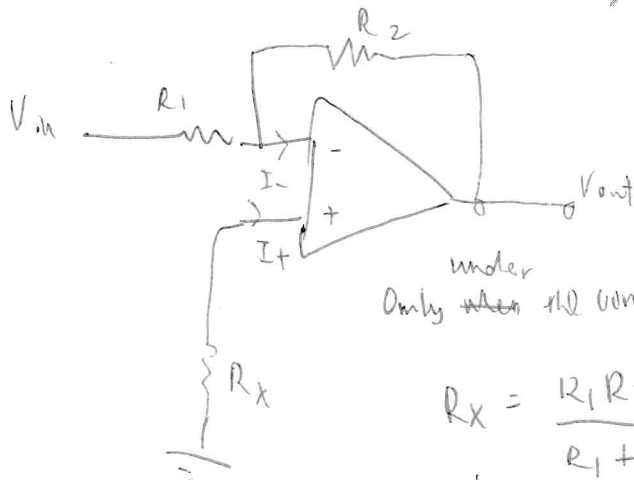


under
only when the condition where

$$I_- = I_+$$

$$R_x = \frac{R_1 R_2}{R_1 + R_2} \quad (R_1 \parallel R_2)$$

→ This formula help to find the value of R_x
so that it can offset the will become zero the

(4)

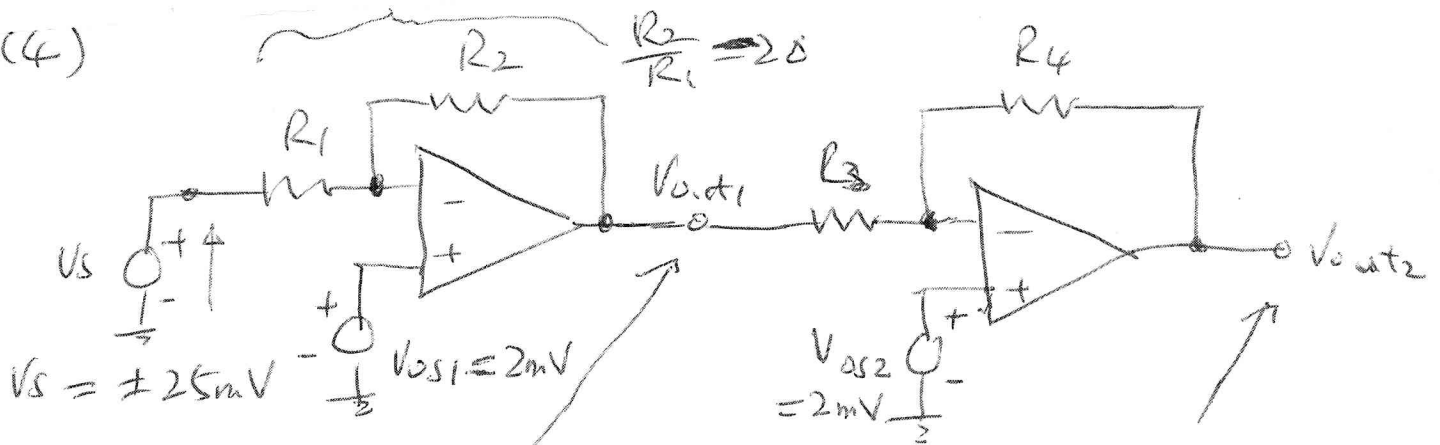

$$V_{out1} = \left(-\frac{R_2}{R_1}\right) V_s + \left(1 + \frac{R_2}{R_1}\right) V_{os1}$$

$$V_{out2} = \left(-\frac{R_4}{R_3}\right) V_{out1} + \left(1 + \frac{R_4}{R_3}\right) V_{os2}$$

$$\therefore V_{out2} = \left(-\frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right) V_s - \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right) V_{os1} + \left(1 + \frac{R_4}{R_3}\right) V_{os2}$$

$$V_{out2} = \left(\frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right) V_s - \left(\frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3}\right) V_{os1} - \left(\frac{R_4}{R_3}\right) V_{os1} + V_{os2} + \left(\frac{R_4}{R_3}\right) V_{os2}$$

If $V_{os1} = V_{os2}$

Worst case happens when $V_s = -25\text{mV}$, $V_{out2} = -14\text{V}$

$$\therefore \left(\frac{R_4}{R_3}\right) = \frac{V_{out2} - V_{os2}}{\left(\frac{R_2}{R_1}\right) (V_s - V_{os1})} =$$

For $V_s = +25\text{mV}$, $V_{out2} = \underline{\underline{+12\text{V}}}$

5(a) $V_{out} = V_p A_{CL} \sin \omega t + \text{dc offset}$

$$\frac{dV_{out}}{dt} = +V_p A_{CL} \omega \cos \omega t = +V_p A_{CL} \cdot 2\pi f \cdot \cos \omega t$$


$$S_R = \left| \frac{dV_{out}}{dt} \right|_{\max} = V_p A_{CL} \cdot 2\pi f_{\max}$$

$$\therefore f_{\max} = \left| \frac{S_R}{V_p \cdot A_{CL} \cdot 2\pi} \right|$$

For $A_{CL} = -50$, $V_p = 0.01 \text{ V}$, $S_R = 1 \text{ V}/\mu\text{s}$

$$\therefore f_{\max} =$$

5(b)

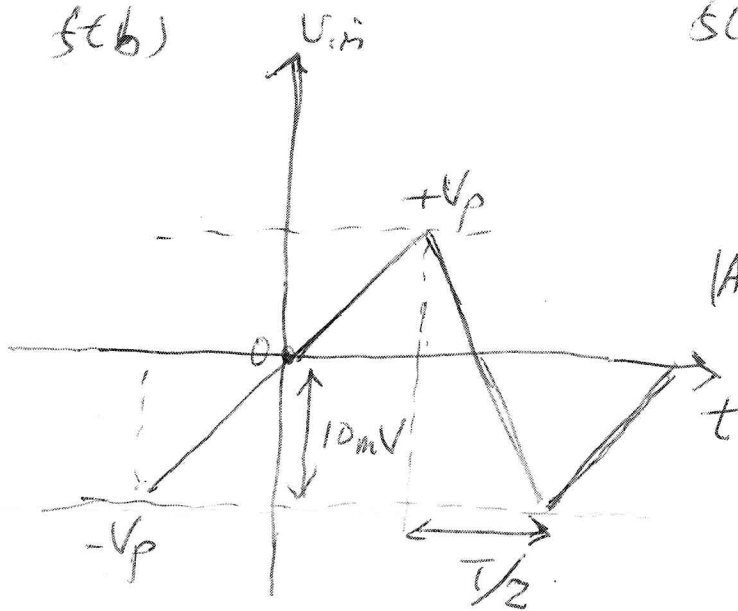


$$|\text{slope}| = \frac{2V_p}{T/2} = \left| \frac{dV_{in}}{dt} \right| = \frac{4V_p}{T}$$

$$\left| \frac{dV_{out}}{dt} \right|_{\max} = 50 \left| \frac{dV_{in}}{dt} \right| \leq S_R = 1 \text{ V}/\mu\text{s} \rightarrow 50 \left(\frac{4V_p}{T} \right) \leq 1 \text{ V}/\mu\text{s}$$

$$f \leq \frac{S_R}{2000V_p} \Rightarrow f_{\max} = \frac{S_R}{2000V_p}$$

$$\therefore f_{\max} = \underline{500 \text{ kHz}}$$

5(c)

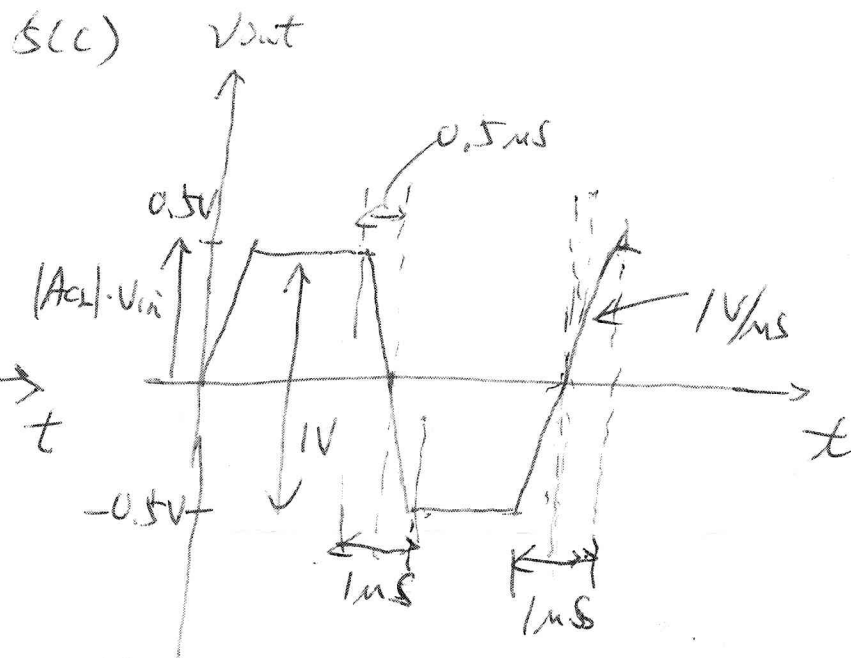

$$A_{CL} = -50$$


0.01 (given)

$$\frac{4V_p}{T} \leq 1 \text{ V}/\mu\text{s} \times 50$$

$$T \leq \frac{4V_p}{1 \text{ V}/\mu\text{s} / 50}$$


$$f \leq \frac{1 \text{ V}/\mu\text{s} / 50}{4(0.01)}$$

6(a)

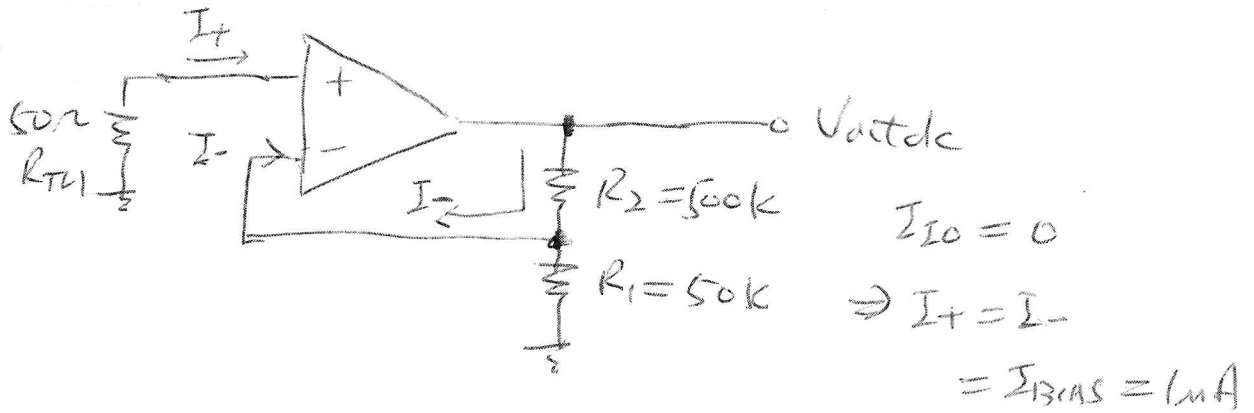

$$V_{outdc} = (-I_+) \cdot R_{TH} - \left(1 + \frac{R_2}{R_1}\right) + (I_-) \cdot R_2$$

6(b)

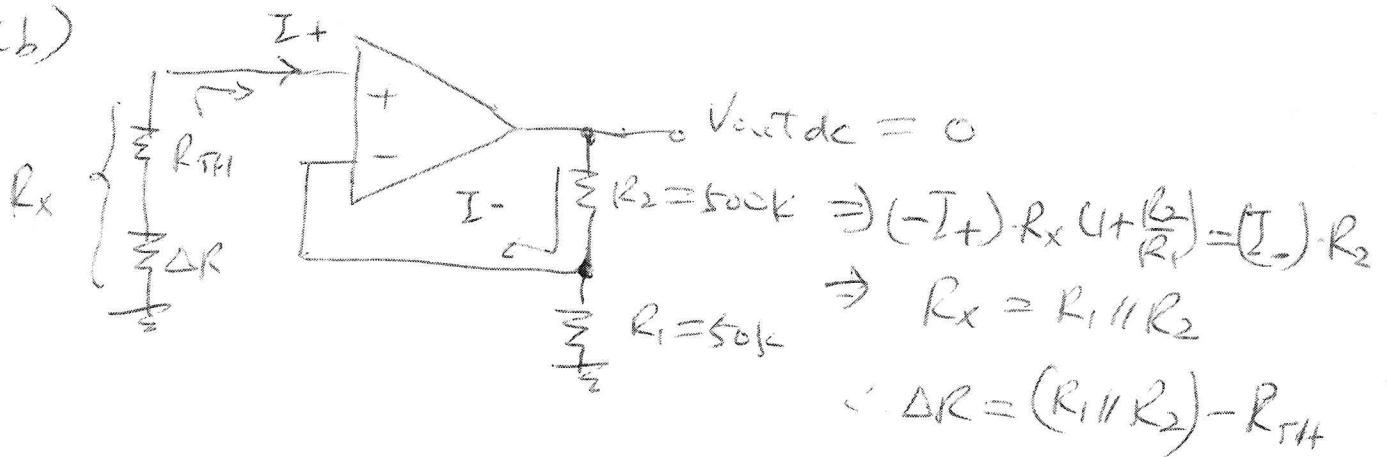

7(a) $A_{CL1} = A_{CL2} = -20$, $V_{sat+} = 14.3V$
 $S_R = 1V/\mu s$, $V_{sat-} = -14V$

$$V_{in} = \frac{V_{out_{twe}}}{|A_{CL1} \cdot A_{CL2}|} = \frac{\pm 14V}{400} = \pm \underline{\underline{35mV}}$$

7(b) $f_{max} = \frac{S_R}{|A_{CL1} \cdot A_{CL2}| \cdot V_p} = \underline{\underline{11.4 KHz}}$