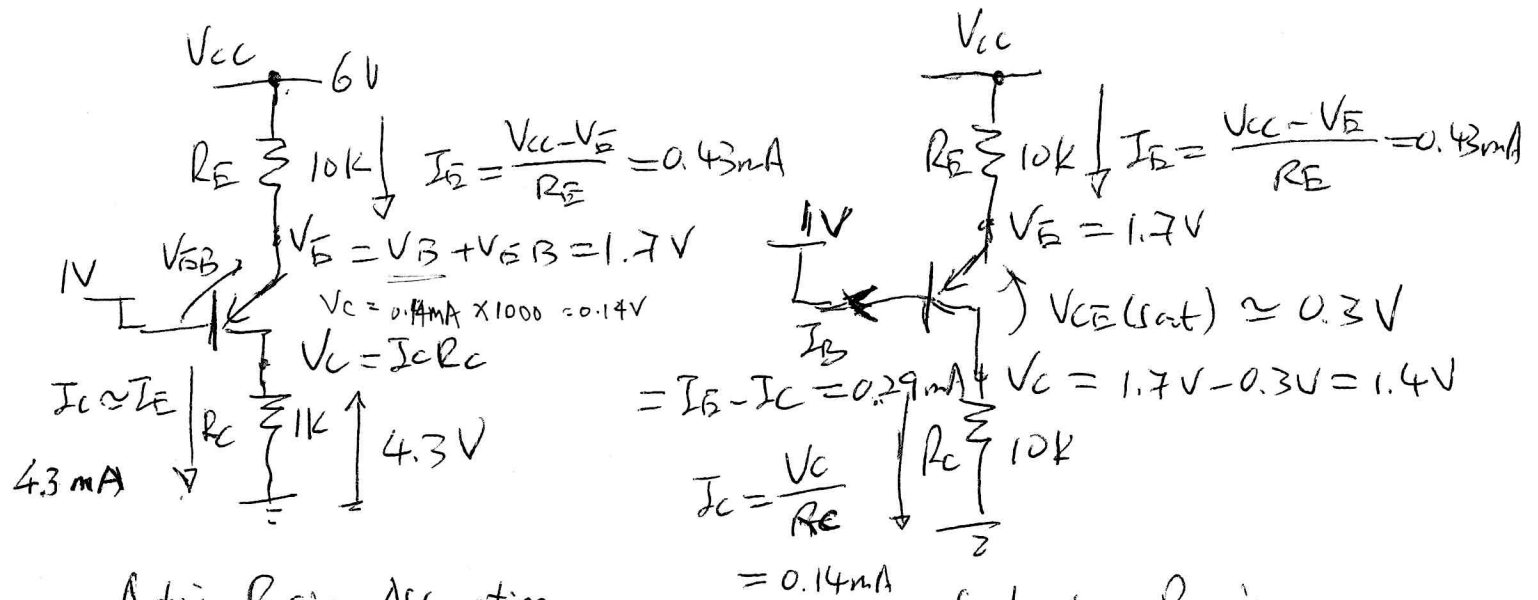


1(a) V_C, V_E, I_B, I_C, I_E ? $V_{EB} = 0.7V$




Active Region Assumption

$\therefore V_C > V_B$, forward biasing in CB junction

Assumption is not correct

Saturation Region

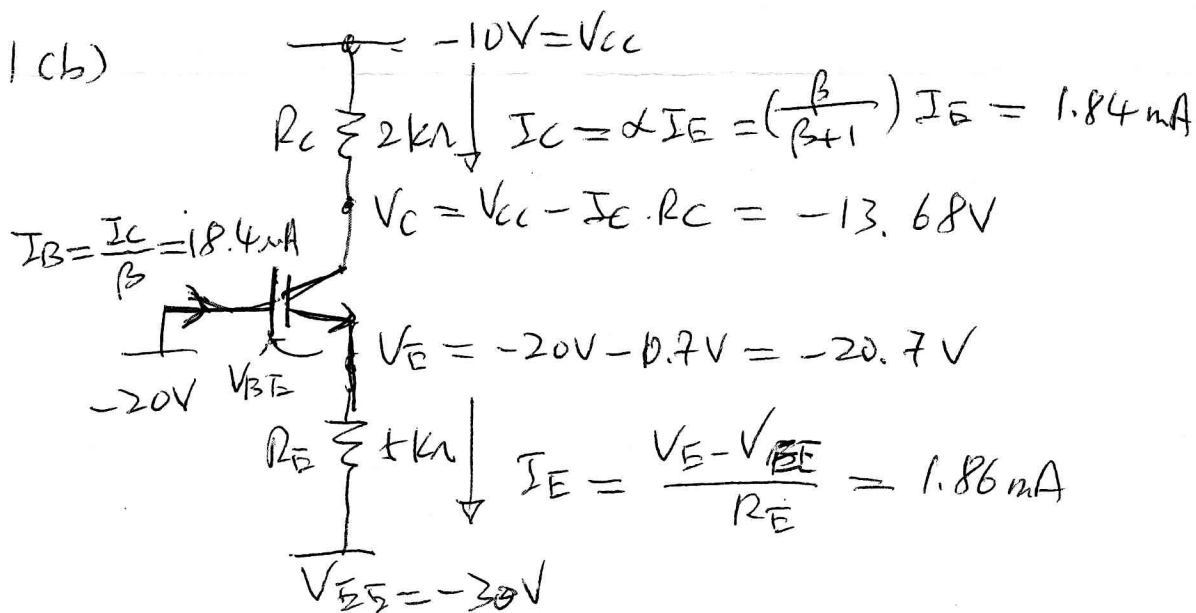

Active Region

$V_{BE} = 0.7V$, $\beta = 100$, $\therefore V_C > V_B$, Q is in active region

2(a) $V_{DD} = +15V$ $V_{GS} + I_D \cdot R_S - 15 = 0$

$$\Rightarrow V_{GS} = 15 - 3 I_D \quad (1)$$

Assume Saturation Region, we have

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 = \frac{0.5}{2} (V_{GS} - 1)^2 \quad (2)$$

(1) into (2), it gives

$$I_D^2 - 9.78 I_D + 21.78 = 0$$

$$\therefore I_D = 6.35 \text{ mA or } 3.43 \text{ mA}$$

For $I_D = 6.35 \text{ mA}$, $V_{GS} = 15 - 3 \times 6.35 = -4.05 \text{ V} < V_{TN}$


$\therefore I_D = 6.35 \text{ mA}$ is rejected

For $I_D = 3.43 \text{ mA}$, $V_{GS} = 4.71 \text{ V} > V_{TN}$

$$\therefore V_{DS} = V_{DD} - I_D \cdot R_D - I_D \cdot R_S - V_{GS} \Rightarrow V_{DS} = 16.28 \text{ V} > V_{GS} - V_{TN}$$

$\therefore$ The operating point is $V_{DS} = 16.28 \text{ V}$, $I_D = 3.43 \text{ mA}$ #

2(b)

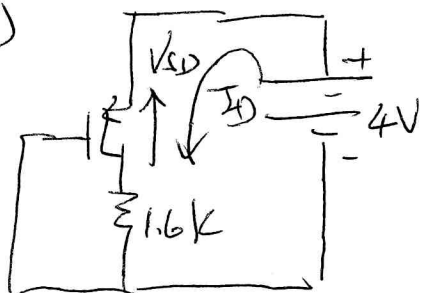

Assume saturation mode

$$I_D = \frac{|K_p|}{2} [(V_{GS}) - |V_{TP}|]^2 = 1.125 \text{ mA}$$

$$\therefore V_{SD} = 4 \text{ V} - I_D \cdot R_S$$

$$= 2.2 \text{ V}$$

$$K_p = -0.25 \text{ mA/V}^2$$

$$V_{TP} = -1 \text{ V}$$

$$V_{SD} = 2.2 \text{ V} < (V_{SG} - |V_{TP}|)$$



$$< (4 - 1) \text{ V}$$

$$< 3 \text{ V}$$

$\therefore$ PMOS is not in saturation region,

it is in triode/ohmic/linear region. #

3

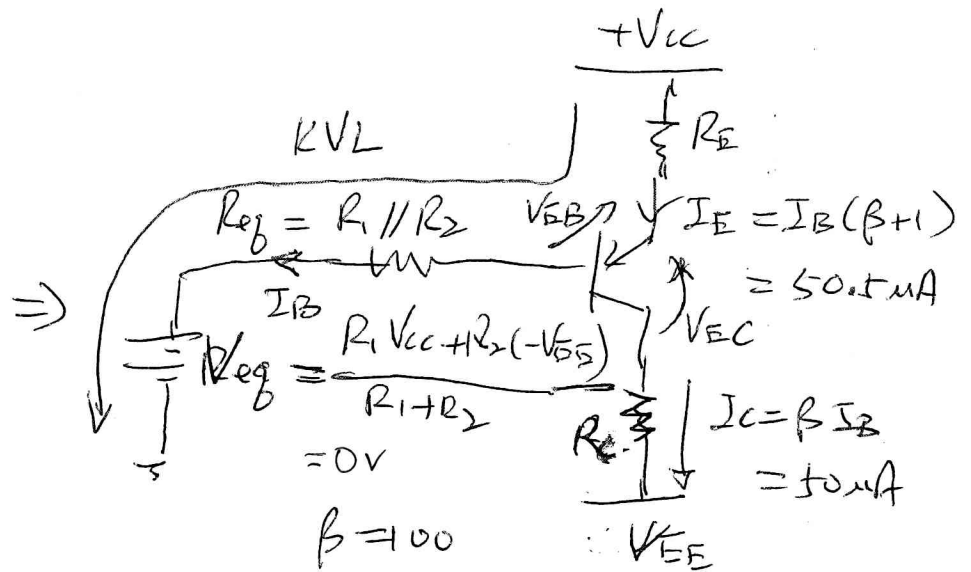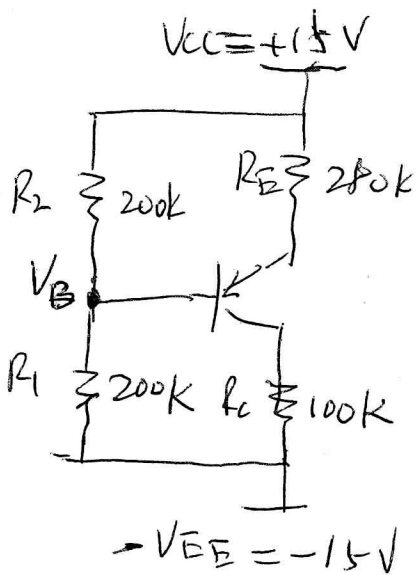

DC Equivalent Circuit (Capacitor Open Circuit)

Alternate Equivalent Circuit

By KVL, $V_{eq} = V_{CC} - (1 + \beta) I_B \cdot R_E - V_{BE} - I_B \cdot R_{eq}$

$\Rightarrow I_B = 0.5 \mu A$


$V_{CE} = V_{CC} - I_E \cdot R_E - I_C \cdot R_C - (-V_{EE}) = 10.86V$

$\therefore$ Q point is $I_E = 50 \mu A$ and $V_{CE} = 10.86V$

Given: $V_B = V_{eq} + I_B \cdot R_{eq} = 0.05V$

Component Power	Value	Source Power	Value
$P_{R1} = \frac{[V_B - (-V_{EE})]^2}{R_1}$	1.13mW	$V_{CC} \times (I_E + I_{R2})$	
$P_{R2} = \frac{(V_{CC} - V_B)^2}{R_2}$	1.12mW	$ V_{EE} (I_C + I_{R1})$	
$P_{RC} = I_C^2 \cdot R_C$	0.25mW	Total Power = 3.76mW	
$P_{RE} = I_E^2 R_E$	0.71mW		
$P_{BJT} = I_C \cdot V_{CE} + I_B \cdot V_{BE} $	0.54mW		

Total Power = 3.75mW

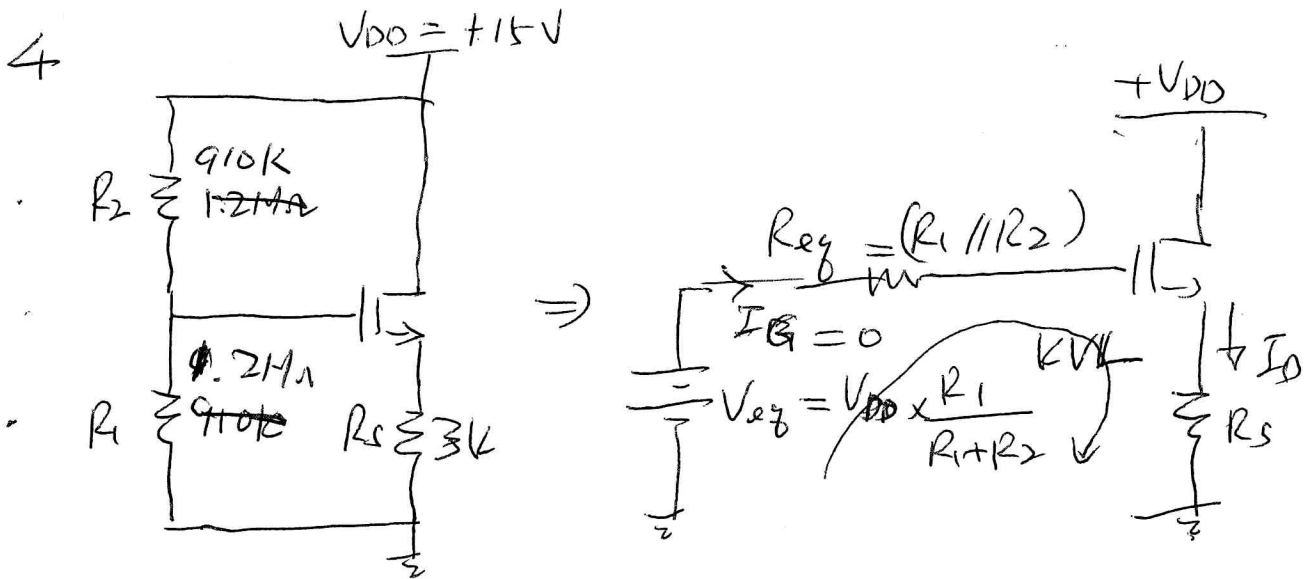

$$K_n = 1mA/V^2$$

By KVL, $V_{GS} = V_{GS} + I_D \cdot R_S$

$$\therefore V_{GS} = 8.53 - 3000 I_D \quad \text{--- (1)}$$

Assume saturation mode

$$I_D = \frac{K_n}{2} (V_{GS} - V_{th})^2 = \frac{0.001}{2} (V_{GS} - 1)^2 \quad \text{--- (2)}$$

(1) into (2) gives

$$4500 I_D^2 - 23.59 I_D + 0.02835 = 0$$

$$\therefore I_D = 1.87mA \text{ or } 3.38mA$$

For $I_D = 3.38mA$, $V_{GS} = 8.53 - 3000 \times 3.38 \times 10^{-3}$
 $= 1.61V (< V_{th})$ (Rejected)

For $I_D = 1.87mA$, $V_{GS} = 2.92V > V_{th}$

and $V_{DS} = V_{DD} - I_D \cdot R_S = 9.39V$

$\therefore$ Q point is $I_D = 1.87mA$ and $V_{DS} = 9.39V$