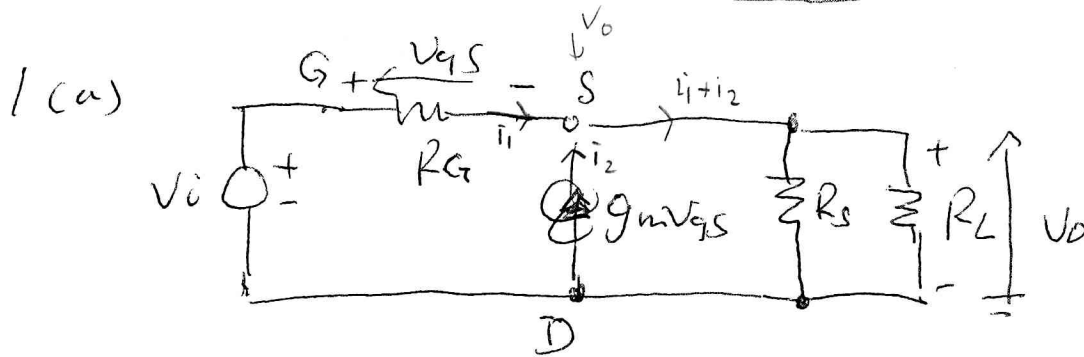




$$g_m = 3.54\text{mS}$$

$r_D$  is ignored

$$R_G = 1\text{M}\Omega$$

$$R_S = 2\text{k}\Omega$$

$$R_L = 100\text{k}\Omega$$

$$V_{DD} = 10\text{V}$$

$$-V_{SS} = -10\text{V}$$

KCL at node S,


$$\frac{V_i - V_o}{R_G} + g_m(V_i - V_o) = \frac{V_o}{R_S \parallel R_L}$$

$$\frac{V_i - V_o}{1 \times 10^6} + 3.54 \times 10^{-3}(V_i - V_o) = \frac{V_o}{1960}$$

$$\Rightarrow V_o = 0.874 V_i$$

$$\therefore A_v = \frac{V_o}{V_i} = \underline{\underline{0.874}}$$
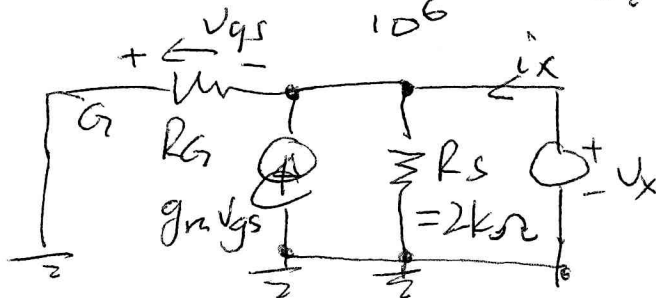
$$R_{in} = \frac{V_i}{i_i} = \frac{V_i}{\frac{V_i - V_o}{10^6}} = \frac{10^6 V_i}{V_i - 0.874 V_i} = \underline{\underline{7.94\text{M}\Omega}}$$




$$V_{GS} = -V_x$$

$$i_x = \frac{V_x}{R_G} + \frac{V_x}{R_S} + g_m V_x = \frac{V_x}{10^6} + \frac{V_x}{2000} + 3.54 \times 10^{-3} V_x$$

$$\therefore R_{out} = \frac{V_x}{i_x} = \underline{\underline{247\Omega}}$$

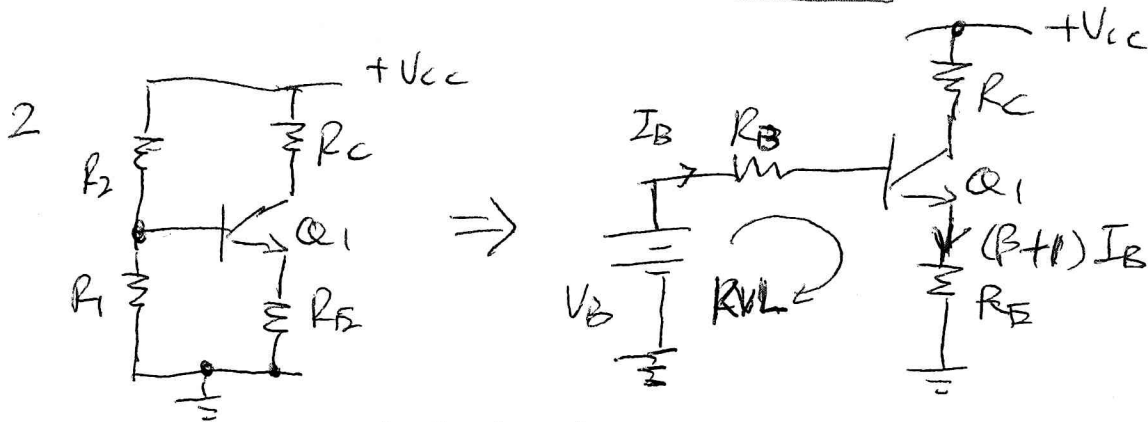1(b) If  $A_v = 1$ ,  $R_{in} \rightarrow \infty$ . #



### DC Analysis

$$V_B = 15 \times \frac{180k}{300k + 180k} = 5.63V, \quad R_B = 300k // 180k = 113k\Omega$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1)R_E} = \frac{5.63 - 0.7}{113k + 101 \times 20k} = 2.31 \mu A$$

$$I_C = \beta I_B = 100 \times 2.31 \mu A = 232 \mu A, \quad I_E = (\beta + 1) I_B = 101 \times 2.31 \mu A$$


$$V_{CE} = V_{DD} - I_C R_C - I_E R_E = 15V - I_C (20k) - I_E (20k) = 5.71V$$

$$\therefore g_m = \frac{I_C}{V_T} = \frac{232 \mu A}{0.025V} = 9.28 mS$$

$$r_{\pi} = \frac{\beta}{g_m} = 10.8 k\Omega$$

$$r_o = \frac{V_A + V_{CE}}{I_C} = \frac{70 + 5.71V}{232 \mu A} = 326 k\Omega$$

# AC analysis

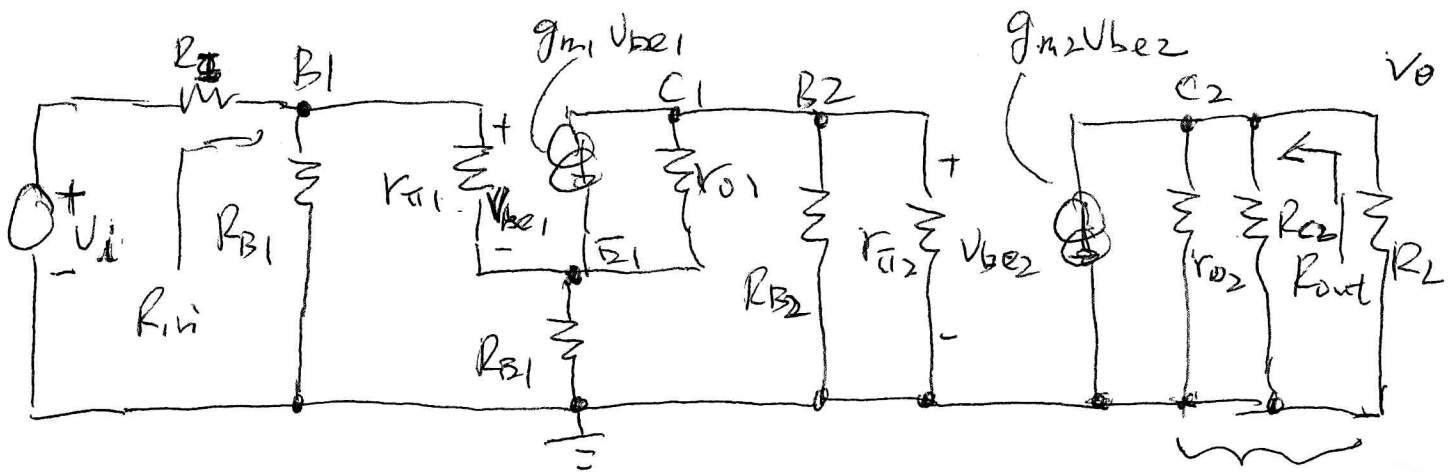

$$R_{B1} = 300k \parallel 180k = 112.5k\Omega$$

$$R_{B2} = 20k \parallel 300k \parallel 180k = 16.98k\Omega$$

$$\therefore R_{in} = R_{B1} \parallel [r_{\pi 1} + (\beta + 1)R_{E1}] = 112.5k \parallel [10.8k + 10(2k)] = 73.6k\Omega$$


$$A_v = \left( \frac{R_{in}}{R_I + R_{in}} \right) \times A_{v1}' \times A_{v2}'$$

$$A_{v1}' = \frac{V_{c1}}{V_{b1}} = \frac{-i_{b1} \cdot \beta_1 (R_{B2} \parallel r_{\pi 2})}{i_{b1} [r_{\pi 1} + (\beta + 1)R_{E1}]} = -3.10 \quad \left( \begin{array}{l} 2k\Omega \text{ in} \\ \text{stage 1 is} \\ \text{not bypassed} \end{array} \right)$$

$$A_{v2}' = \frac{V_o}{V_{b2}} = \frac{-g_{m2} V_{be2} R_L'}{V_{be2}} = -g_{m2} R_L' = -147$$


$$\text{where } R_L' = r_{o2} \parallel R_{C2} \parallel R_L = 326k \parallel 20k \parallel 100k$$
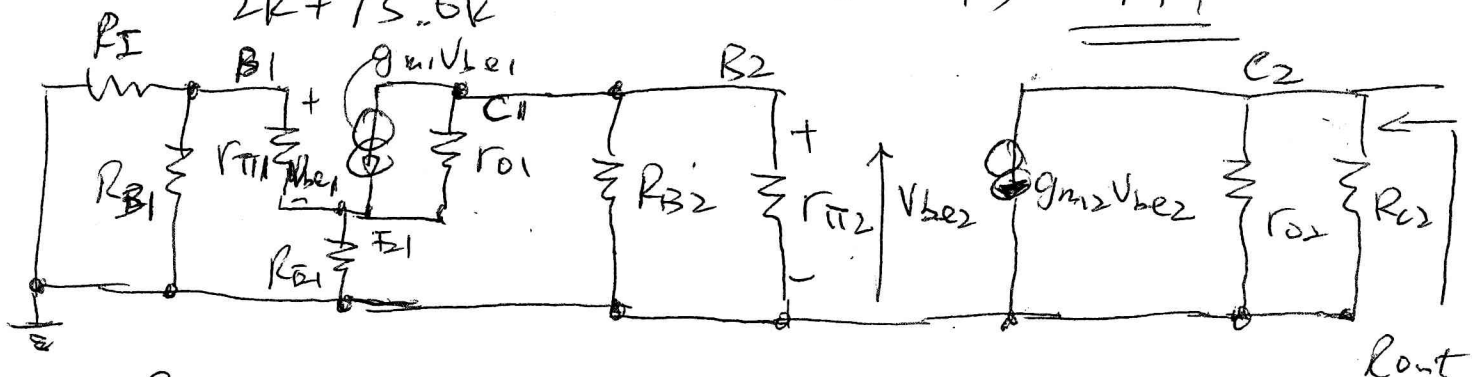
$$\therefore A_v = \frac{73.6k}{2k + 73.6k} \times (-3.10) \times (-147) = 444$$



$$R_{out} = 20k \parallel r_{o2} = 20k \parallel 326k = 18.8k\Omega$$

3

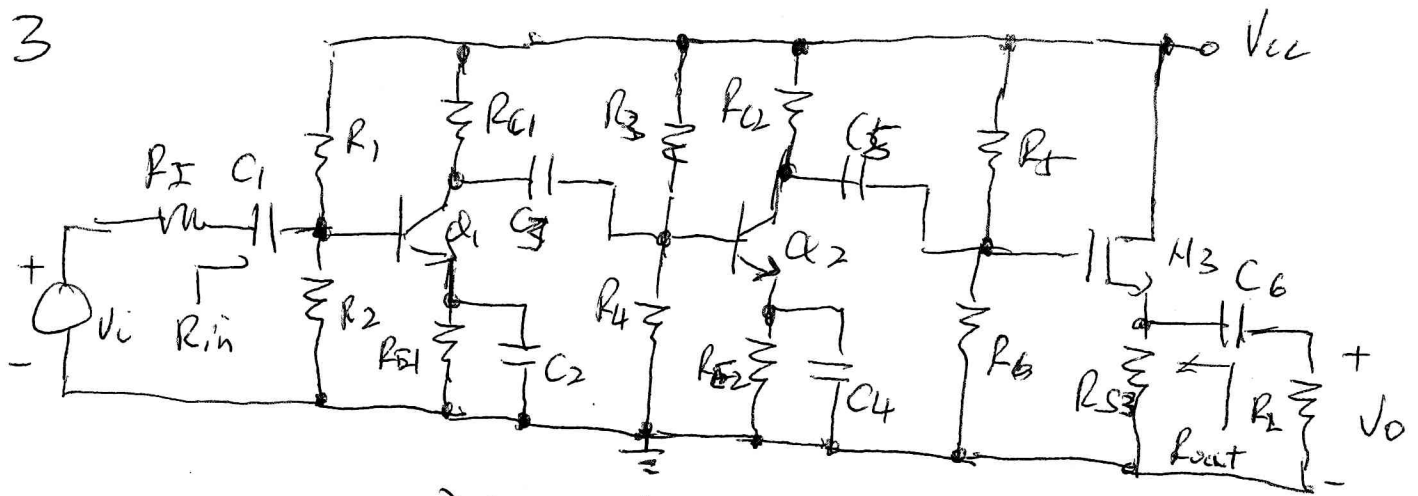

### DC analysis

| Q1                         | Q2                         | M3                    |
|----------------------------|----------------------------|-----------------------|
| $V_{B1}, R_{B1}$           | $V_{B2}, R_{B2}$           | See Q5 of Tutorial 5. |
| $I_{C1}, V_{CE1}$          | $I_{C2}, V_{CE2}$          |                       |
| $g_{m1}, r_{\pi1}, r_{o1}$ | $g_{m2}, r_{\pi2}, r_{o2}$ |                       |

Note:  $I_C = \frac{\beta(V_B - V_{BE})}{R_B + (\beta + 1)R_E}$ ,  $V_{CE} = V_{CC} - I_C R_C - I_E R_E$   
 $= V_{CC} - I_C \left( R_C + \frac{R_E}{\alpha} \right)$

$$R_{in} = R_{B1} \parallel r_{\pi1}$$

$$A_v = \left( \frac{R_{in}}{R_i + R_{in}} \right) \times A_{v1}' \times A_{v2}' \times A_{v3}'$$

$A_{v1}'$  and  $A_{v2}'$  are the ac gain of stage 1 & stage 2 CE amplifiers with full-bypassed emitter resistor.

$A_{v3}'$  is the ac gain of common drain amplifier (same as Q2 of Tutorial 6)

$$R_{out} = r_{o3} \parallel R_{S3} \parallel \frac{1}{g_{m3}}$$

### Input signal range

M3

$$(1) \quad V_{GS3} \leq 0.2(V_{GS3} - V_{TN3})$$

$$(2) \quad \text{Relate } V_i \text{ and } V_{GS3}$$

$$(3) \quad \text{Find the worst case } V_i$$

Q2

$$V_{BE2} \leq 0.005 V$$

$$\text{Relate } V_i \text{ \& } V_{BE2}$$