
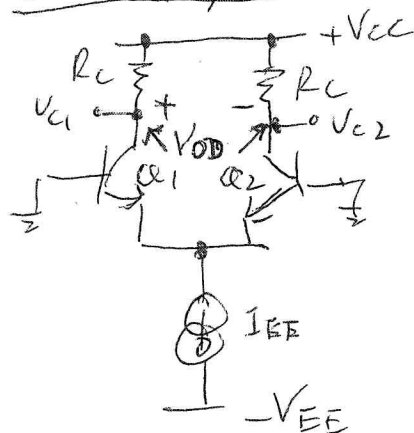


EE2002 Tutorial 8

(a) DC Analysis

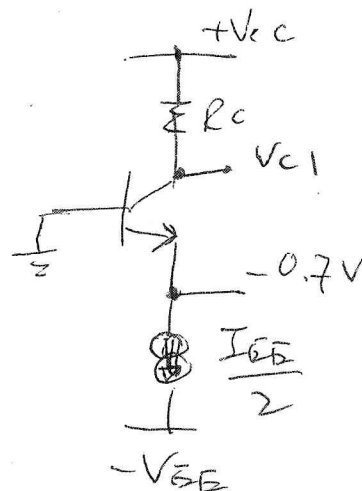

DC half circuit



$$I_C = \alpha I_E = \alpha \frac{I_{EE}}{2} = \left(\frac{\beta}{\beta + 1} \right) \frac{I_{EE}}{2} = \frac{100}{101} \times \frac{400 \mu A}{2} = 198 \mu A$$

$$V_{CE} = V_{CC} - I_C R_C - (-0.7V) = 12 - 39K \times 198 \mu A - (-0.7) = 4.98V$$


∴ Q point is 198μA and 4.98V

(b) $g_m = \frac{I_C}{nV_T} = 40 \cdot I_C = 7.92mS$ where $nV_T = 25mV$


Differential-Mode Analysis

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{7.92m} = 12.6K\Omega$$
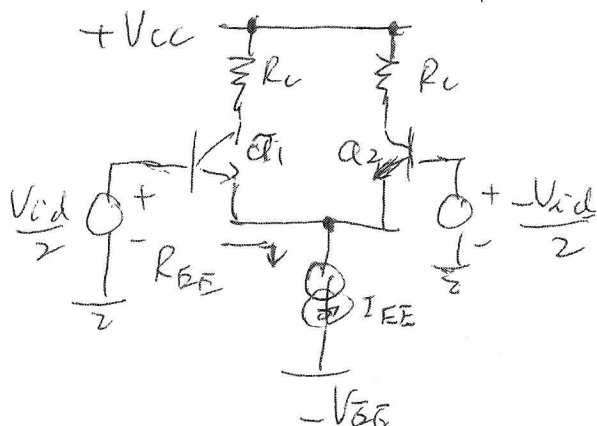
$$r_o = \infty, \text{ for } V_A = \infty$$



Differential-mode half circuit

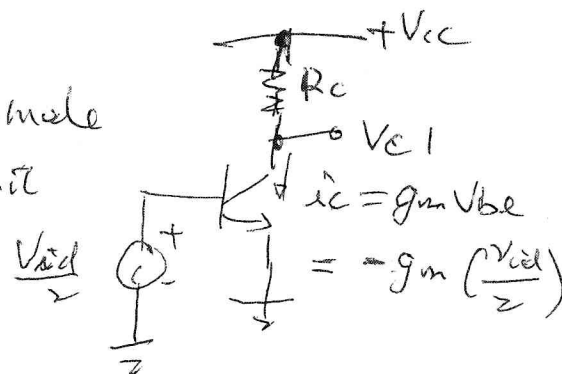


$$V_{C1} = -g_m \left(\frac{V_{id}}{2} \right) R_C, \quad V_{C2} = g_m \left(\frac{V_{id}}{2} \right) R_C$$

$$V_{od} = V_{C1} - V_{C2} = -g_m V_{id} R_C$$


$$A_{m_diff} = \frac{V_{od}}{V_{id}} = -g_m R_C = -7.92m \times 39k = -309$$

$$A_{m_se1} = \frac{V_{c1}}{V_{id}} = \frac{-g_m R_C}{2} = -154.5$$


$$R_{id} = 2r_{\pi} = 25.2k\Omega$$

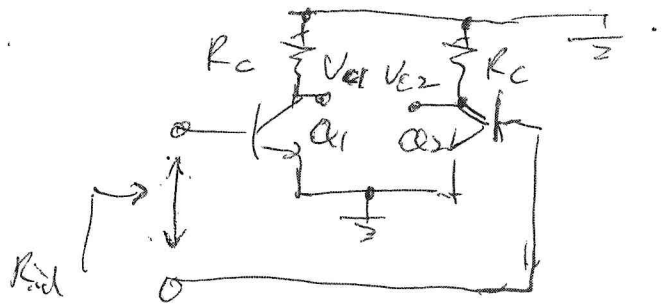

Common-Mode Analysis

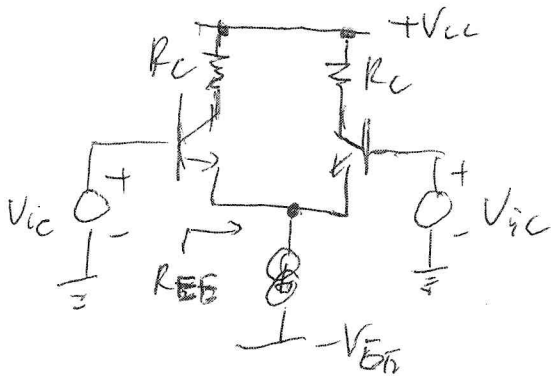


Common-Mode
Half Circuit
 $\Rightarrow$

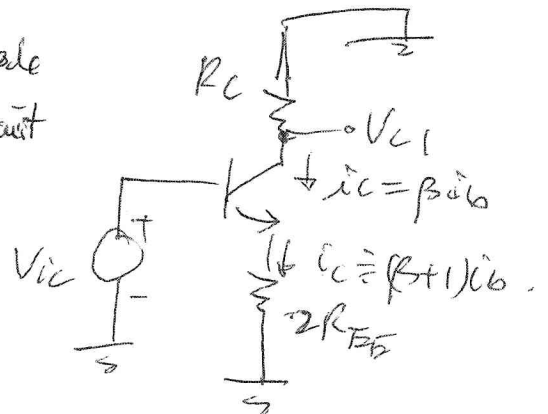

$\therefore V_{od} = V_{c1} - V_{c2} = 0$, Therefore, $A_{m_diff} = 0$

$$A_{m_se1} = \frac{V_{c1}}{V_{ic}} = \frac{-\beta i_b R_C}{i_b [r_{\pi} + (\beta + 1) 2R_{EE}]} = -0.0965$$
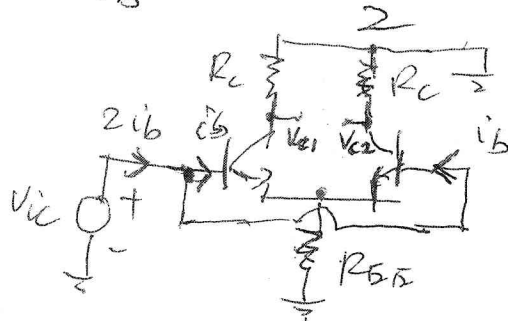
$$R_{ic} = \frac{V_{ic}}{i_{b1} + i_{b2}} = \frac{V_{ic}}{2i_b} = \frac{r_{\pi} + (\beta + 1) 2R_{EE}}{2} = 20.2M\Omega$$



CNRR at differential output

$$CNRR = \frac{A_{m_diff}}{A_{m_se1}} = \frac{-309}{0} = \infty$$

CNRR at single-ended output


$$CNRR = \frac{A_{m_se1}}{A_{m_se1}} = \frac{-154.5}{-0.0965}$$

$$= 1600 \text{ or } 64.1 \text{ dB}$$


output resistance: $R_{o1} = R_{o2} = r_{o1} \parallel R_C = 39k\Omega$

$$R_{od} = R_{o1} + R_{o2} = 2R_C = 78k\Omega \quad -2-$$

2(a) DC Analysis

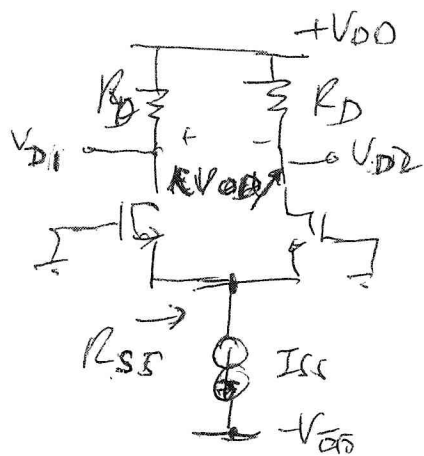

DC half circuit
 $\Rightarrow$

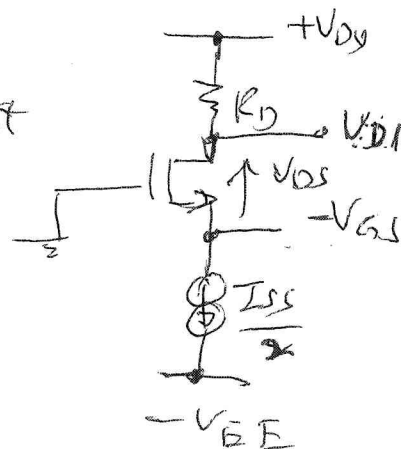

$$I_D = \frac{I_{SS}}{2} = 150 \mu A, \quad V_{GS} = V_{TN} + \sqrt{\frac{2I_D}{K_n}} = 1.866 V$$



$$V_{DS} = V_{DD} - I_D \times R_D - (-V_{GS}) = 5.62 V$$

$$\therefore V_{DS} = 5.62 > V_{GS} - V_{TN} = 0.866 V$$

The MOSFETs are in saturation region

$$2(b) \quad g_m = \sqrt{2K_n I_D} = 0.346 \text{ mS}$$

Differential-Mode Analysis

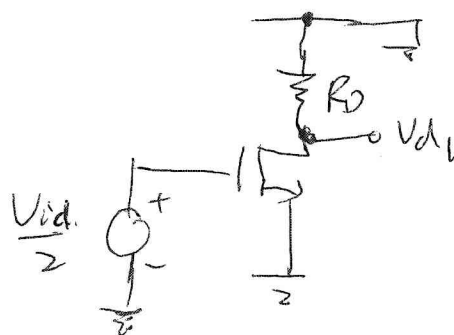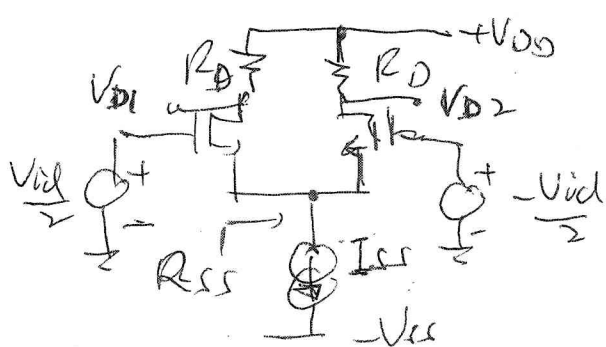

$$V_{d1} = -g_m \left(\frac{V_{id}}{2} \right) R_D, \quad V_{d2} = -g_m \left(-\frac{V_{id}}{2} \right) R_D$$


$$V_{od} = V_{d1} - V_{d2} = -g_m V_{id} R_D$$

$$\therefore A_{dm-diff} = \frac{V_{od}}{V_{id}} = -0.346 \text{ m} \times 75 \text{ k} = -26$$


$$A_{d-sel} = \frac{V_{d1}}{V_{id}} = \frac{-g_m R_D}{2} = \frac{-26}{2} = -13$$

$$R_{id} = \infty$$

Common-Mode Analysis

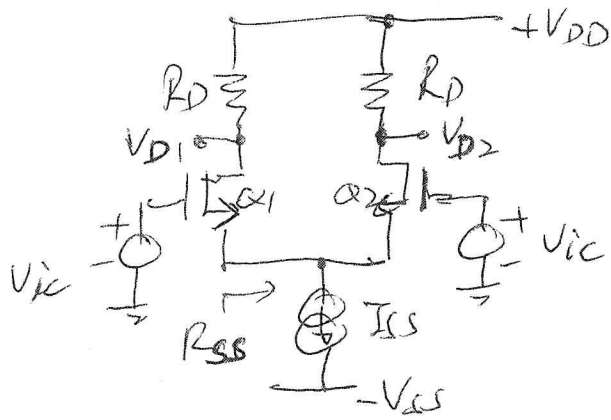

Common-Mode
half circuit

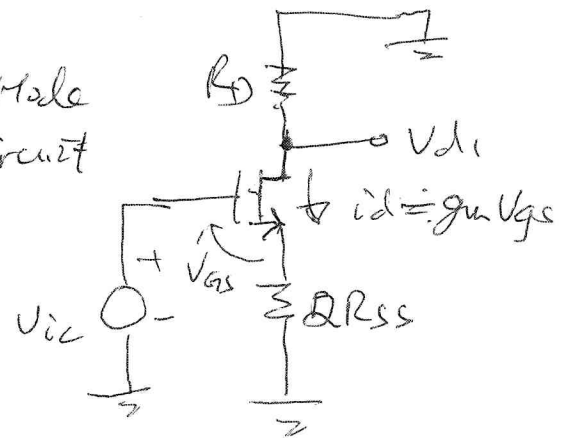

$$\therefore V_{od} = V_{d1} - V_{d2} = 0, \therefore A_{cm-diff} = 0$$

$$A_{cm-se1} = \frac{V_{d1}}{V_{ic}} = \frac{-g_m V_{gs} R_D}{V_{gs} + g_m V_{gs} (2R_{ss})} = \frac{-g_m R_D}{1 + 2g_m R_{ss}} = -0.232$$

$$R_{ic} = \infty$$

CMRR

Differential Output

$$CMRR = \left| \frac{-26}{0} \right| = \infty$$

Single-Ended Output



$$CMRR = \left| \frac{-13}{-0.232} \right| = 56 \text{ or } 35 \text{ dB}$$

Output Resistances

$$R_{o1} = R_{o2} = R_D \parallel r_o \approx R_D = 75 \text{ k}\Omega$$

$$R_{o2} = 2(R_D \parallel r_o) \approx 2R_D = 150 \text{ k}\Omega$$

3(a) DC Analysis

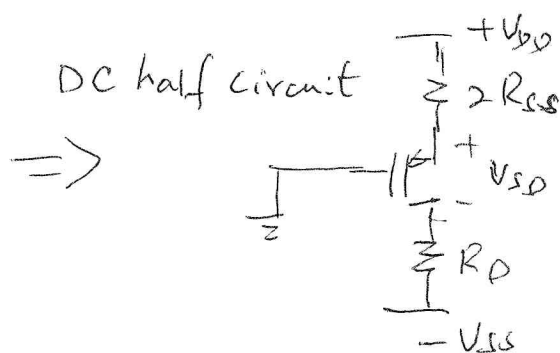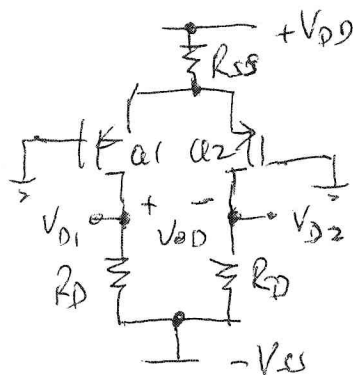

$$I_D = \frac{18 - V_{SG}}{2 \times 56k} \Rightarrow 11.2 V_{SG}^2 - 21.4 V_{SG} - 6.8 = 0$$


$$\therefore V_{SG} = +2.19V \text{ or } V_{SG} = -0.28V \text{ (rejected)}$$

$$\therefore I_D = \frac{18 - V_{SG}}{112k} \approx 141 \mu A$$


$$\text{and } V_{SD} = V_{SG} - I_D R_D - (-V_{SS}) = 2.19 - 141 \mu A \times 91k + 18 = 7.34V$$

$$3(b) \quad g_m = \sqrt{2|k_p|I_D} = \sqrt{2 \times (2 \times 10^{-4}) \times (1.41 \times 10^{-4})} = 0.237 \text{ mS}$$

Differential-Mode Analysis

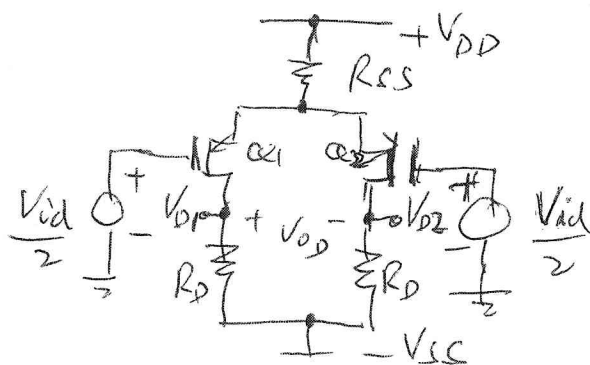

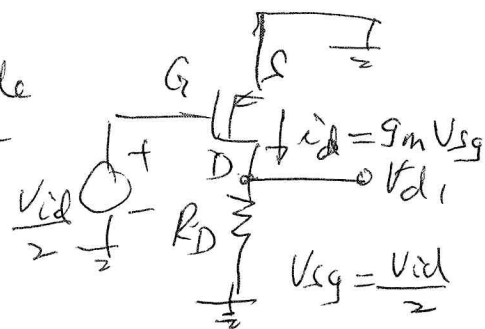Differential-Mode
half circuit $\Rightarrow$




$$V_{D1} = -g_m \left(\frac{V_{id}}{2} \right) R_D, \quad V_{D2} = -g_m \left(-\frac{V_{id}}{2} \right) R_D$$

$$\therefore V_{OD} = V_{D1} - V_{D2} = -g_m V_{id} R_D$$


$$\therefore A_{dm-diff} = \frac{V_{OD}}{V_{id}} = -g_m R_D = -0.237 \text{ m} \times 91k = -21.57$$

$$A_{dm-se1} = \frac{A_{dm-diff}}{2} = -10.78, \quad R_{ic} = \infty$$

Common-Mode Analysis

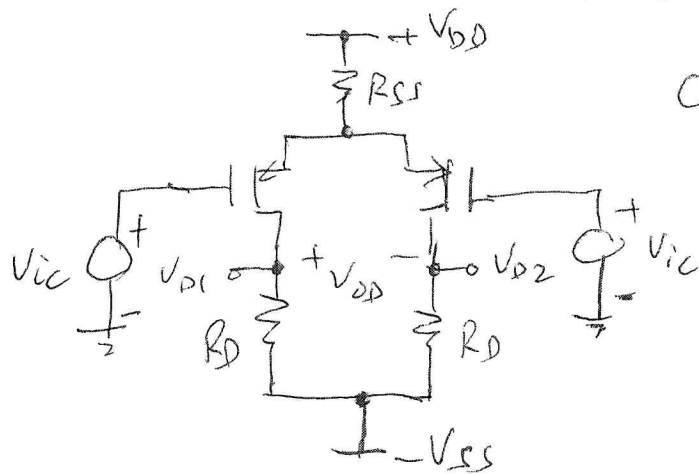

Common-Mode
half circuit

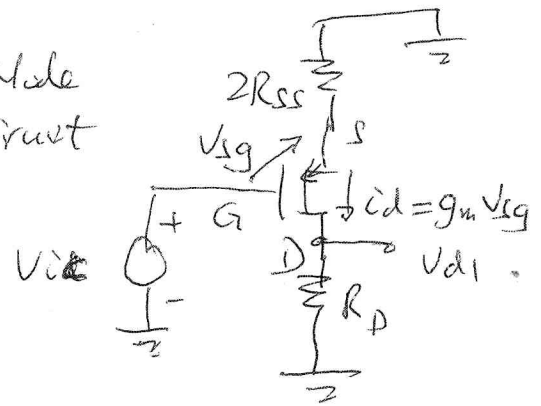

Since $V_{od} = V_{o1} - V_{o2} = 0$, $\Rightarrow A_{cm-diff} = 0$

$$A_{cm-sel} = \frac{V_{o1}}{V_{ic}} = \frac{-g_m V_{sg} R_D}{V_{sg} + g_m V_{sg} (2R_{SS})} = \frac{-g_m R_D}{1 + 2g_m R_{SS}} = \underline{\underline{-0.783}}$$

$$R_{ic} = \infty$$

CMRR

Differential output

$$CMRR = \left| \frac{-21.57}{0} \right| = \infty$$

Single-Ended output

$$CMRR = \left| \frac{-10.78}{0.78} \right| = 13.82 \text{ or } 22.81 \text{ dB}$$

Output Resistance

$$R_{o1} = R_{o2} = R_D \parallel r_{o2} \approx R_D \approx 91 \text{ k}\Omega$$

$$R_{od} = 2(R_D \parallel r_o) \approx 2R_D = 182 \text{ k}\Omega$$